

Experiment 2.2

Wheatstone Bridge

Justin B, Aditya D

October 23, 2019

Table of Contents

1	Objectives	1
2	Experimental Results	1
3	Discussion	1
4	Conclusion	1
	References	2

1 Objectives

2 Experimental Results

As labeled in Figure 12 [1], the following values were chosen:

$$E = 12.0V$$

$$R_1 = 100\Omega$$

$$R_2 = 910\Omega$$

$$R_3 = 0 - 200\Omega$$

$$R_x = 960.7\Omega$$

The 200Ω potentiometer was chosen because the bridge is balanced when it has a resistance of 106Ω , allowing for maximal variation.

Force (N)	Voltage (V)
1.226	0.167
1.275	0.176
1.271	0.182
1.238	0.180
1.245	0.176

Table 1: Force versus Voltage across bridge

3 Discussion

4 Conclusion

References

- [1] N. Dimopoulos, F. Gebali, *Laboratory Manual: ECE 250, Linear Circuits I (Edition 4)*, University of Victoria, Victoria, B.C, 2018.